

Jason Weiser
Session: 022
ENGR ID: jweiser
UCR NetID: jweis012@ucr.edu

Lab 2


Video Checkoff link:

<https://drive.google.com/drive/folders/1Cpb5T16FBCyPflKHGQP3RjBh4zqX86X?usp=sharing>


Summary:

This lab dealt with creating layouts and running DRC/LVS simulations. We did it with an inverter and a NAND gate. The inverter was left over from Lab 1, but the NAND gate was a new setup. I learned about carefully following each design rule and about how wiring transistors carries over between levels of abstractions. It was also a chance to internalize what low level gates in circuits actually do.

INVERTER Layout

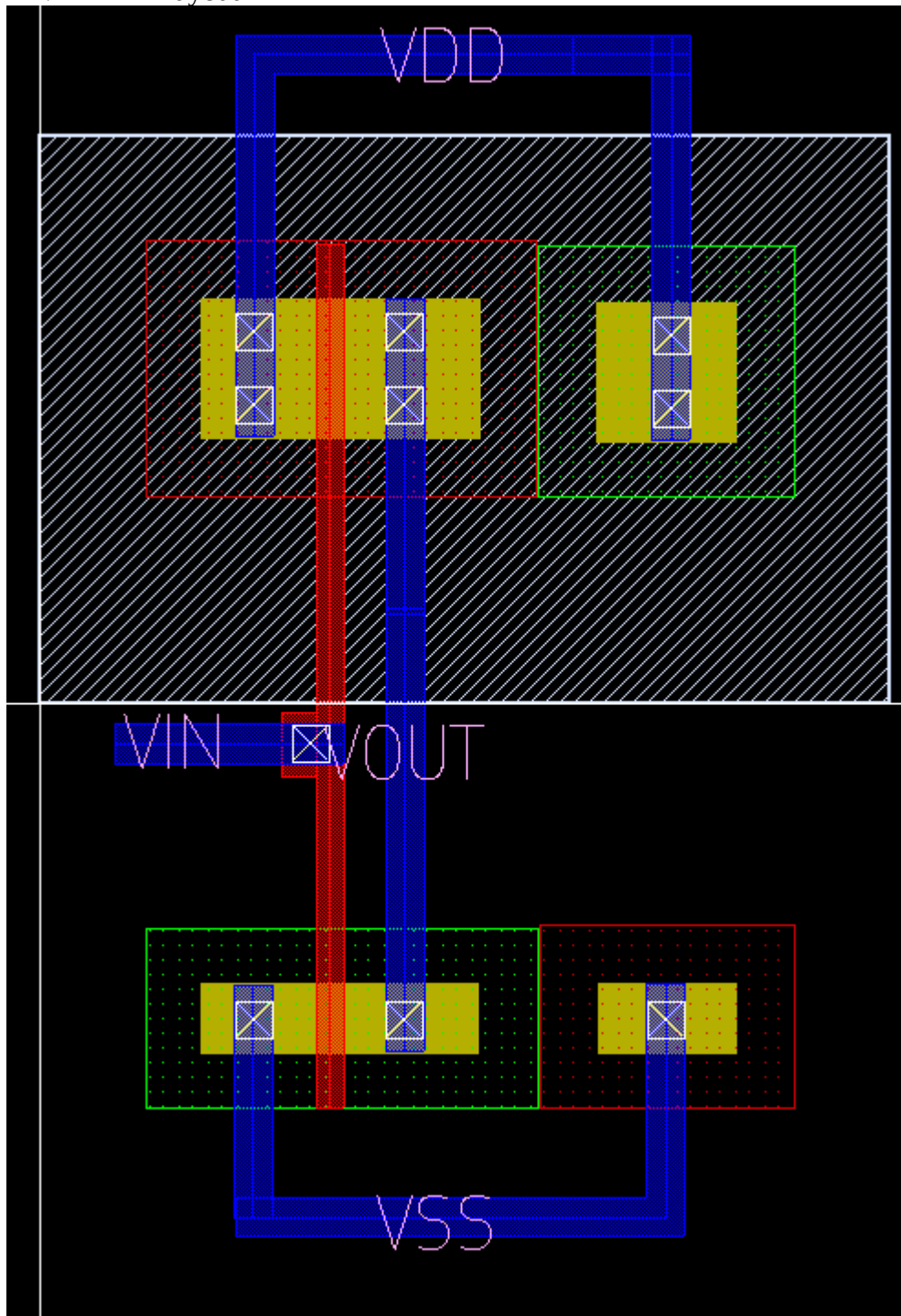

INVERTER DRC

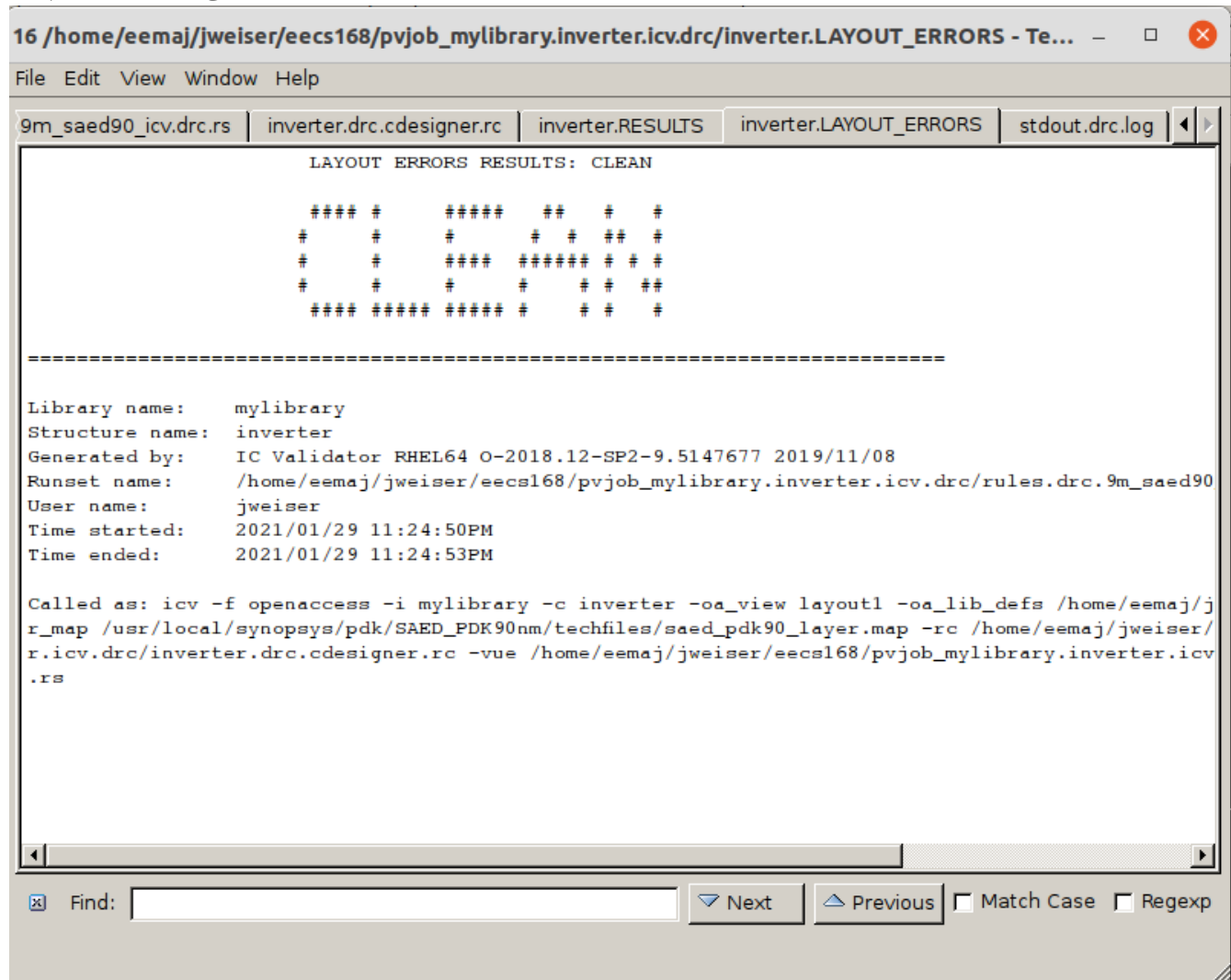

The screenshot shows a terminal window titled "16 /home/eemaj/jweiser/eecs168/pvjob_mylibrary.inverter.icv.drc/inverter.LAYOUT_ERRORS - Te...". The window has a menu bar with "File", "Edit", "View", "Window", and "Help". Below the menu bar is a tab bar with five tabs: "9m_saed90_icv.drc.rs", "inverter.drc.cdesigner.rc", "inverter.RESULTS", "inverter.LAYOUT_ERRORS" (which is the active tab), and "stdout.drc.log". The main content area displays the following text:

```
LAYOUT_ERRORS_RESULTS: CLEAN

#####
#           #####   ##   #   #
#   #       #       #   #   ##  #
#   #       #####   ##### #   #
#   #       #       #   #   ##  #
##### #####   ##### #   #   #

=====

Library name:      mylibrary
Structure name:    inverter
Generated by:      IC Validator RHEL64 O-2018.12-SP2-9.5147677 2019/11/08
Runset name:       /home/eemaj/jweiser/eecs168/pvjob_mylibrary.inverter.icv.drc/rules.drc.9m_saed90
User name:         jweiser
Time started:      2021/01/29 11:24:50PM
Time ended:        2021/01/29 11:24:53PM

Called as: icv -f openaccess -i mylibrary -c inverter -oa_view layout1 -oa_lib_defs /home/eemaj/j
r_map /usr/local/synopsys/pdk/SAED_PDK90nm/techfiles/saed_pdk90_layer.map -rc /home/eemaj/jweiser/
r.icv.drc/inverter.drc.cdesigner.rc -vue /home/eemaj/jweiser/eecs168/pvjob_mylibrary.inverter.icv
.rs
```

At the bottom of the window is a search bar with a "Find:" label, a text input field, and buttons for "Next", "Previous", "Match Case", and "Regexp".

INVERTER LVS

TOP BLOCK COMPARE RESULTS

PASS

[inverter, inverter]

Model: intel(R) Xeon(R) Silver 4214 CPU @ 2.20GHz

Netlist Extraction Statistics

Library name: mylibrary
Structure name: inverter
Generated by: IC Validator RHEL64 0-2018.12-SP2-9.5147677 2019/11/08
Runset name: /home/eemaj/jweiser/eecs168/pvjob_mylibrary.inverter.icv.lvs/rules.lvs.9m_saed90_lvs.lvs.rs
User name: jweiser
Time started: 2021/01/29 11:26:33PM
Time ended: 2021/01/29 11:26:37PM

Called as: icv -f openaccess -i mylibrary -c inverter -oa_view layout1 -oa_lib_defs /home/eemaj/jweiser/eecs168/lib.defs -oa_layer_map /usr/local/synopsys/pdk/SAED_PDK90nm/tech1


Layout vs. Schematic Statistics

Schematic: /home/eemaj/jweiser/eecs168/pvjob_mylibrary.inverter.icv.lvs/inverter.sch_out


LVS Errors:

1 successful equivalencies
0 failed equivalencies


NAND SCHEMATIC

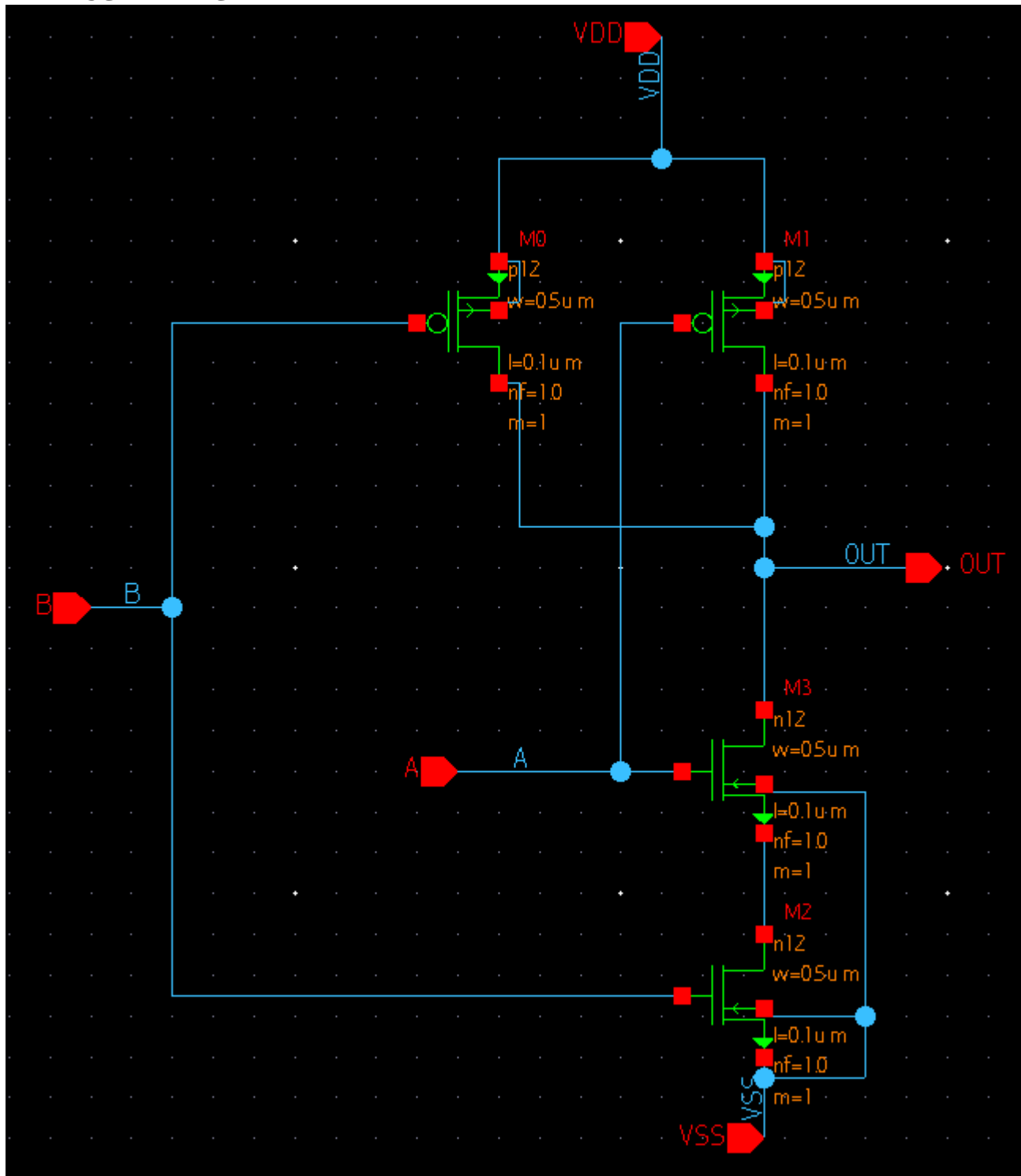


NAND Test Bench Schematic

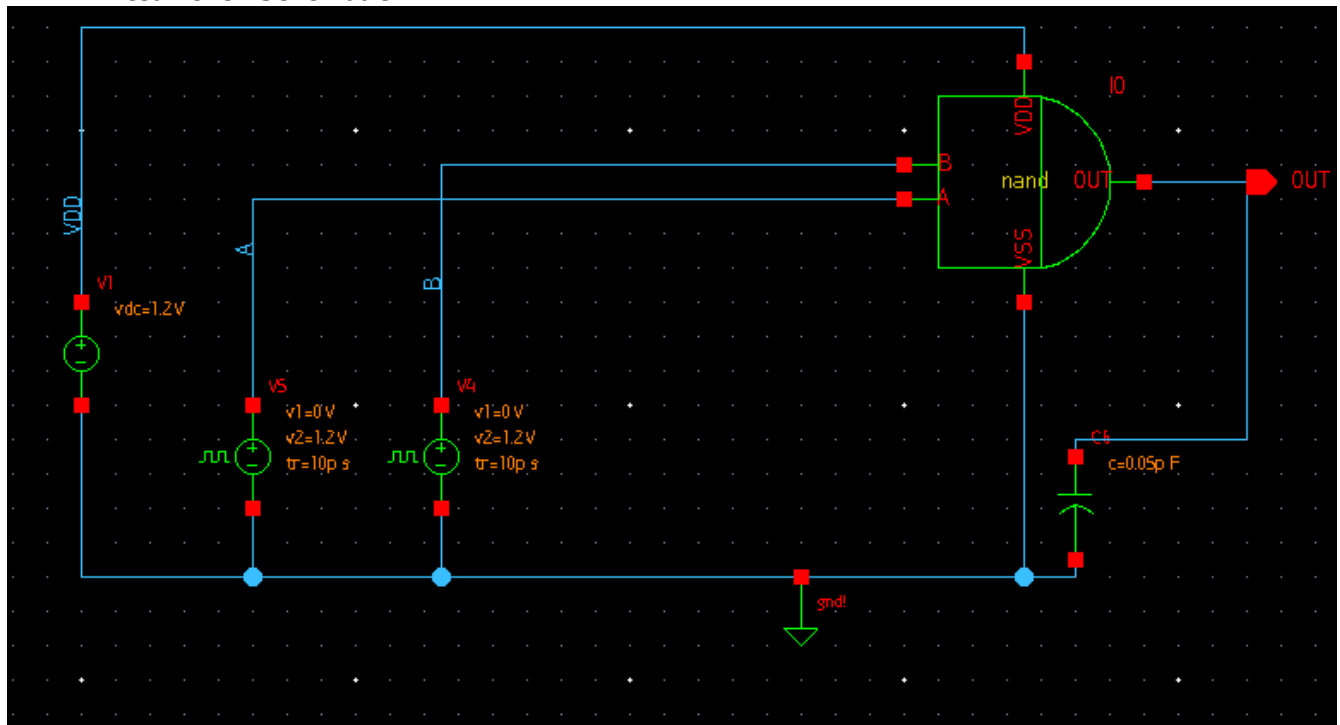

NAND Test Bench Results

 

NAND LAYOUT

 

NAND DRC

```
21 /home/eemaj/jweiser/eecs168/pvjob_mylibrary.nand.icv.drc/nand.LAYOUT_ERRORS - Text Vie...
File Edit View Window Help

rules.drc.9m_saed90_icv.drc.rs | nand.drc.cdesigner.rc | nand.RESULTS | nand.LAYOUT_ERRORS | stdout.drc.log |

LAYOUT_ERRORS_RESULTS: CLEAN


#####
#           #####  ##  #  #
#   #       #   #   #  ## #
#   #       #####  #  #
#   #       #   #   #  ##
#####

=====

Library name:      mylibrary
Structure name:    nand
Generated by:      IC Validator RHEL64 O-2018.12-SP2-9.5147677 2019/11/08
Runset name:       /home/eemaj/jweiser/eecs168/pvjob_mylibrary.nand.icv.drc/rules.drc.9m_saed90_icv
User name:         jweiser
Time started:      2021/01/29 11:29:49PM
Time ended:        2021/01/29 11:29:51PM

Called as: icv -f openaccess -i mylibrary -c nand -oa_view layout1 -oa_lib_defs /home/eemaj/jweiser/
p /usr/local/synopsys/pdk/SAED_PDK90nm/techfiles/saed_pdk90_layer.map -rc /home/eemaj/jweiser/eecs
c/nand.drc.cdesigner.rc -vue /home/eemaj/jweiser/eecs168/pvjob_mylibrary.nand.icv.drc/rules.drc.9
```


NAND LVS

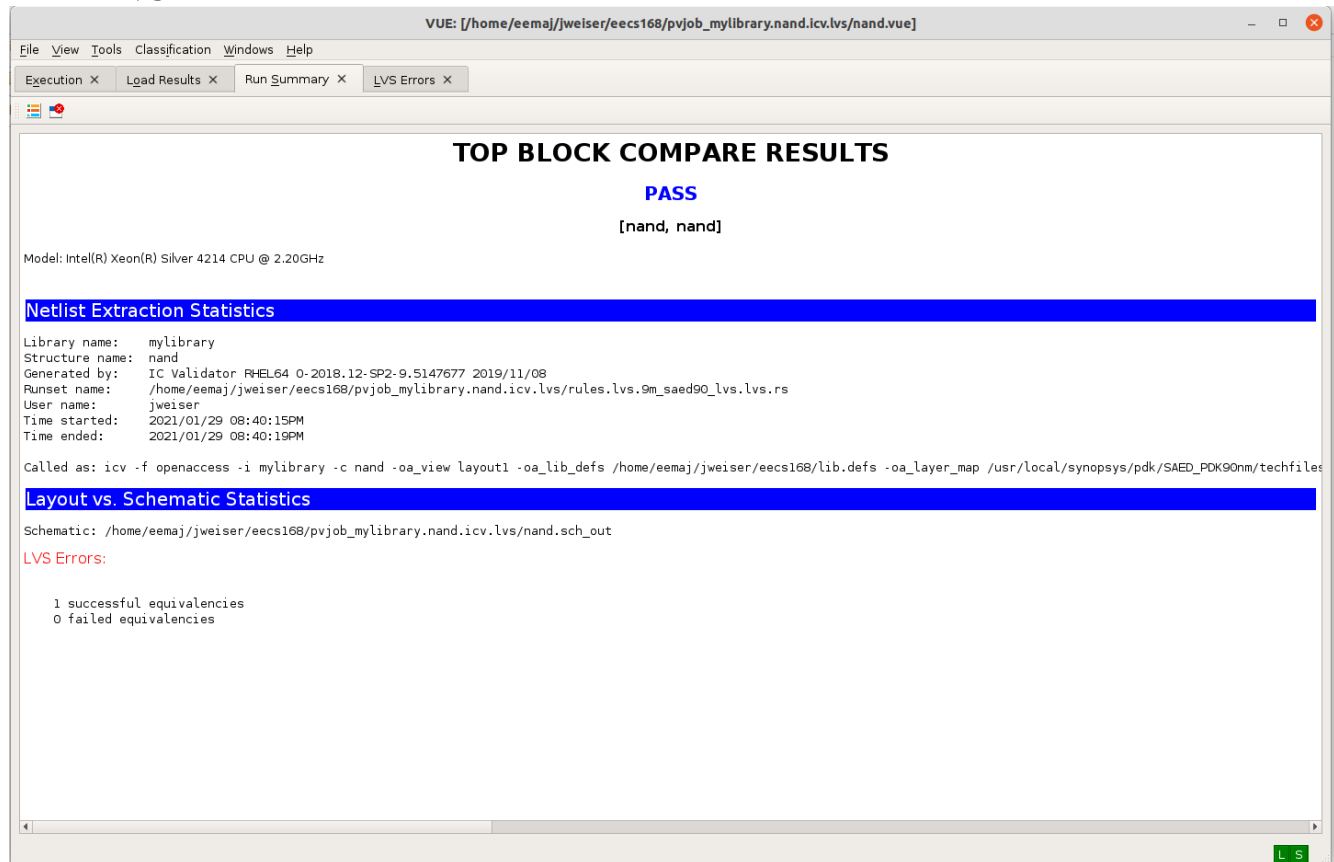

Issues:

I had an issue with matching names on the NAND gate because I didn't share connections on the wires of the bottom 2 gates for the schematic. I had trouble with the NAND test bench parameters. General unfamiliarity and learning was also a challenge.